

De-coupling

Once you get more than a handful of active components together you need to de-couple the power supply. What this is, and why, is described here.


INTRODUCTION **DE-COUPLING** PROTECTION POWER POWER EXAMPLES
 POWER SUPPLIES PWM LEDS INPUTS ARRAYS MERGING CODE
 STATE MACHINE



De-coupling

When an otherwise good design works, but is erratic, unreliable or just goes crazy then nine time out of ten it is the power supply de-coupling. And you will find that the tenth time, turns out to be power supply de-coupling as well. So what is it, and why is it needed?

Basically when an integrated circuit works it works by switching current on and off. This switching happens very rapidly. Each time the current changes the voltage changes as well. This is because of the fact that everything has a resistance, even wire and copper traces on a printed circuit board have resistance. It's not a very big resistance but it doesn't have to be. A changing current passing through a resistance will produce a changing voltage across it. Now consider a chain of several ICs being powered:-

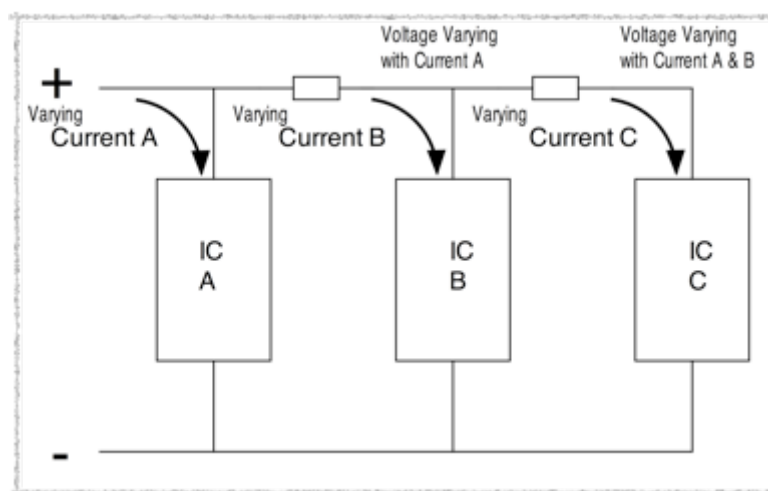

As the current changes in ICA the voltage supplying that IC also changes, what is worse the voltage supplying all the ICs changes. But it gets worse, as ICB works it's current changes and that also causes the voltage to vary on the other ICs and so on. In fact the voltage supplying the ICs is changing very rapidly due to the contribution of all the ICs in the circuit. The switching in an IC happens very rapidly so this voltage variation is very rapid or at a high frequency. The more rapid the circuit switches the higher the frequency of this voltage variation on the power supply, this is

called noise. Things can get so bad that the noise can stop a circuit from functioning correctly. It is to get rid of this noise that we have to de-couple the power supply. Essentially getting rid of the noise is easy, at least conceptually simply put a capacitor across the supply to smooth out the supply or filter the noise out.



Practicalities

If you look at the frequency spectrum of this noise you will find that it has a wide range so you might think it is easy to filter it out, just use a large capacitor.

Unfortunately it is not as easy as that. A capacitor looks like a low resistance for high frequencies, the higher the frequency the lower it looks. The capacitive reactance (or X_c) is the name we give to the resistance of a capacitor for an alternating signal. It is given by this formula:-

$$X_c = \frac{1}{2\pi fC}$$

Where F is the frequency in Hz C is the capacitance in Farads. So a practical first approximation to a solution is use a 0.1uF capacitor like this one across the supply of each chip. It is much much better than nothing.

Don't just ignore that formula, look at it for a moment. It is a reciprocal, that is it is one over something. This means that the bigger things are on the bottom of the fraction the smaller the other side of the equation gets. But while it can get small it will never get to zero. You will see the bigger the capacitance the more of a short it look like, also the higher the frequency the more of a short it look like. Great so all we need to do is put in a big capacitor and that will remove all the high frequencies. Well sorry no life is a bit more complex than that.


Inductance

As well as everything, like wires, having a resistance they also have an inductance. That is everything acts like a coil as well. An inductor is the reverse of a capacitor, It looks like a very high resistance to an alternating signal. The effective resistance is called the inductive reactance (or X_L) and is given by:-

$$X_L = 2\pi fL$$

Where F is the frequency in Hz L is the inductance in Henrys.

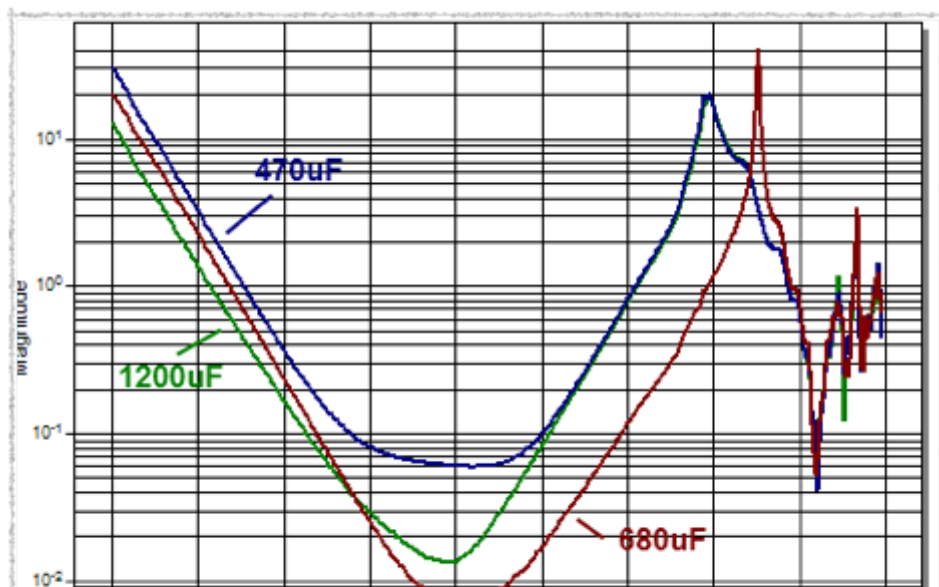Note that it is very similar to the capacitive reactance only its not a reciprocal. That means the bigger the frequency and inductance gets the higher the effective resistance is. Here is a plot of reactance against frequency for some real capacitors with a large values.






filters noise up to a certain frequency. This is known as the “self resonant” frequency of a capacitor at at any frequency above its self resonance the component looks like an inductor and is doing nothing to remove noise from the supply.


You will see from the graph above it is not always the largest or smallest capacitor that has the best high frequency effect.

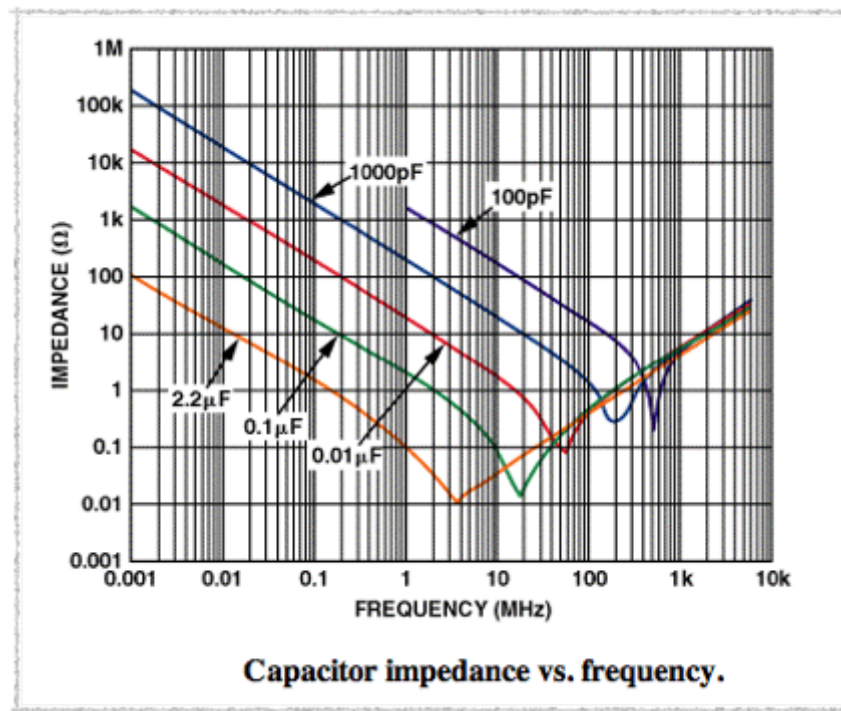The graph below shows both capacitive and inductive reactance for several different values of capacitor but all having an inductance of 1nH. These are theoretical curves.




In the case of large electrolytic capacitors a high inductance is produced due to the way it is built, as a sandwich of metal foil and insulator, all rolled up, this is a lot like a coil. However for small ceramic capacitors the biggest cause of inductance is the components leads. To maximise the effects these must be as short as possible.

For effective supply de-coupling that frequency has to cover as wide a range as possible and certainly the range of noise being generated by the circuits. So this is why we often see two different values of capacitor used in parallel. One large one to filter out the low frequency variations and a small on for the high frequency noise. Typical values are 47μF and 0.1μF or 0.01μF (10nF) and as low frequency variations are system wide you tend to need only one large capacitor. However, high frequency noise is no so easily suppressed and so you tend to need a small capacitor on every, or every other chip. The type of capacitor construction that produces the lowest inductance is the ceramic type and those are always used for the smaller capacitors. The lead from the circuit board to the capacitor body can produce a lot of inductance so it is important that this is as short as possible. Surface mounting capacitors are ideal in this respect and are to be preferred if practical. Modern IC designs often have the positive supply and ground pinned out next to each other to make this de-coupling especially effective.

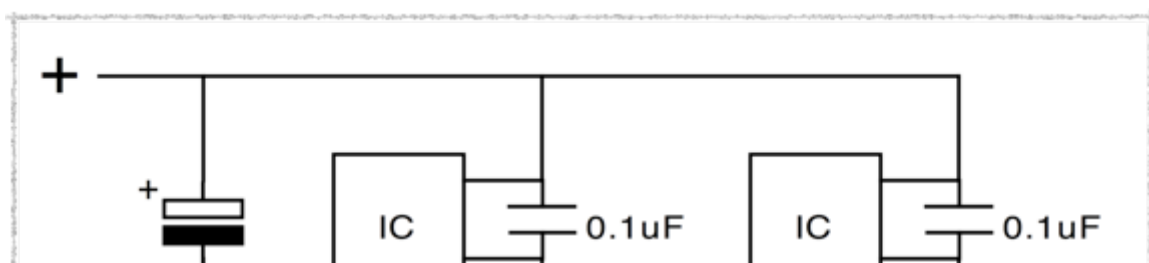




The way this is drawn indicates that the capacitors are close to the IC and the supply is fed to the capacitor before being passed on to the IC. For smaller circuits you would probably get away with a de-coupling capacitor every other IC but professionals do de-couple every IC. In general I try to aim at at least half the number of de-coupling capacitors as ICs and if there is an especially heavy current IC I will often throw in another large electrolytic.

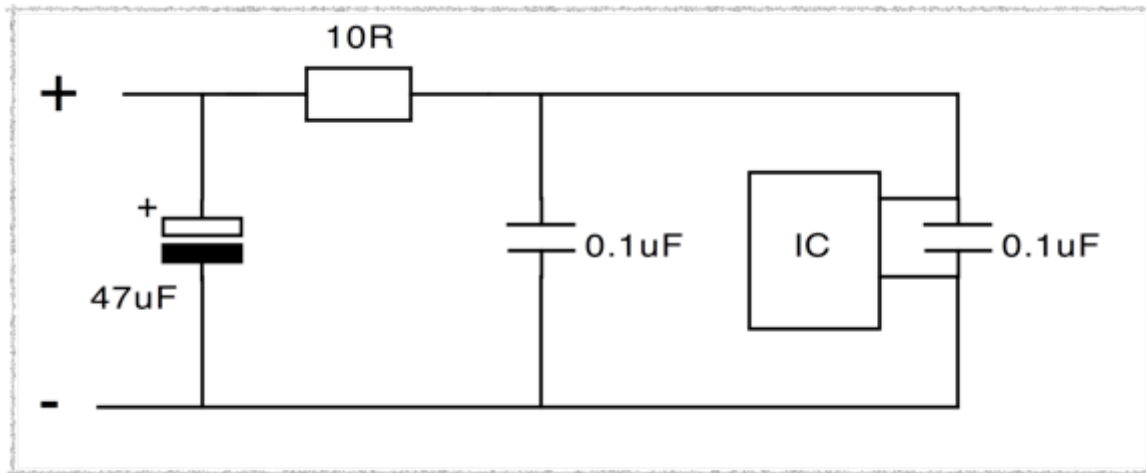

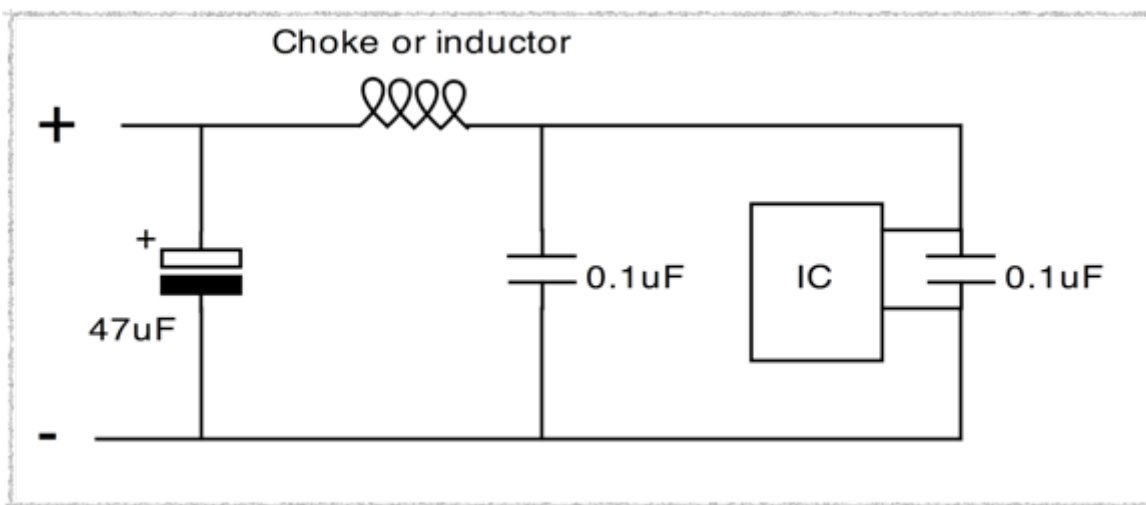There are occasions when you require more isolation with particularly sensitive circuits like oscillators or A/D converters for example. Here I would use a series resistor to boost the isolation for that chip alone. This helps to isolate it from the rest of the chain.



This has the disadvantage of reducing the supply impedance and increasing the noise for heavy currents. For the ultimate in de-coupling use a small choke or inductor as well. The inductance value is not too critical, but generally as big as you can manage, a few tens of mill Henrys is normal. This is useful if the load generates a lot of noise. Not only does this protect the load from noise it also prevents noise generated by the load from getting into the rest of the circuit. This arrangement would be especially suited to the case where the load was not an IC but a motor. Motors can generate so much noise on the supply that a single one can cause circuits to fail. Larger capacitors after the choke can also help in those situations. As motors draw a lot of current these can often be several hundred micro Farads.

